


## Energy Harvest Board Voltage plot

### 1. Case Study: Harvester with output voltage > VIN


Set up:

- 1) Given 3.3V power source, connect 3 diodes (100V 15A R-6) in series to decrease the input voltage(Solar In) to 3.0V.
- 2) Connect the 3.0V power source to Solar In and the voltage on Solar In get 1.887V
- 3) Before connect energy harvest board to battery, the EXT BAT get 1.734V
- 4) After connect energy harvest board to battery, the EXT BAT get 3.3V

Plot in document:

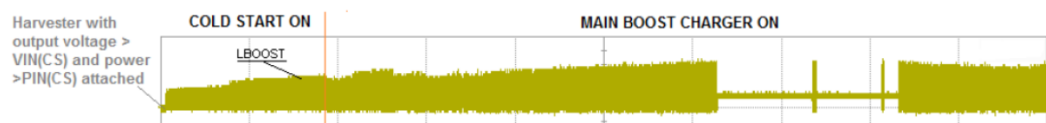

Data collected from 30 mins testing:

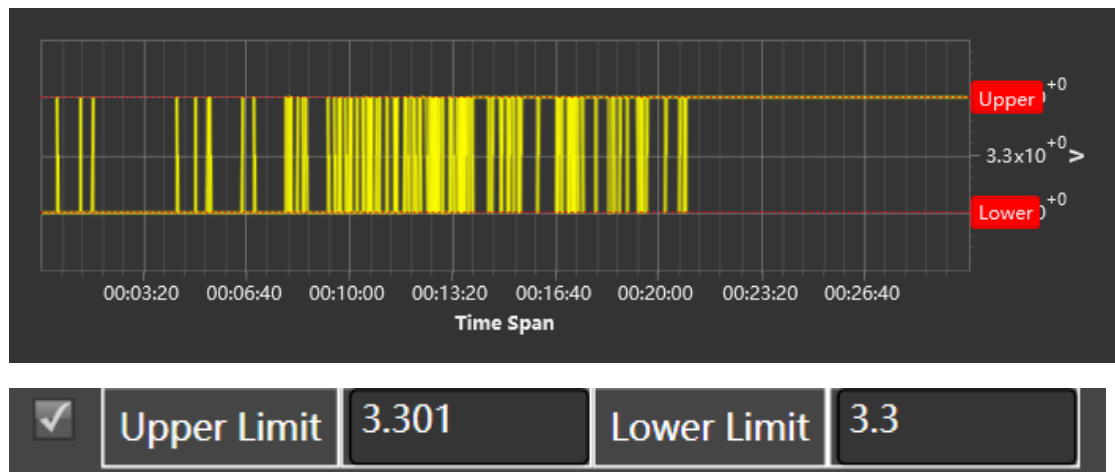


### 2. Case study: V Bat plot for charging


Set up:

- 1) Given 3.3V power source and connected it to Solar In.
- 2) Before connect battery, EXT BAT get 3.979 V.
- 3) After connect battery, EXT BAT get 3.668V at beginning.

Plot in document:

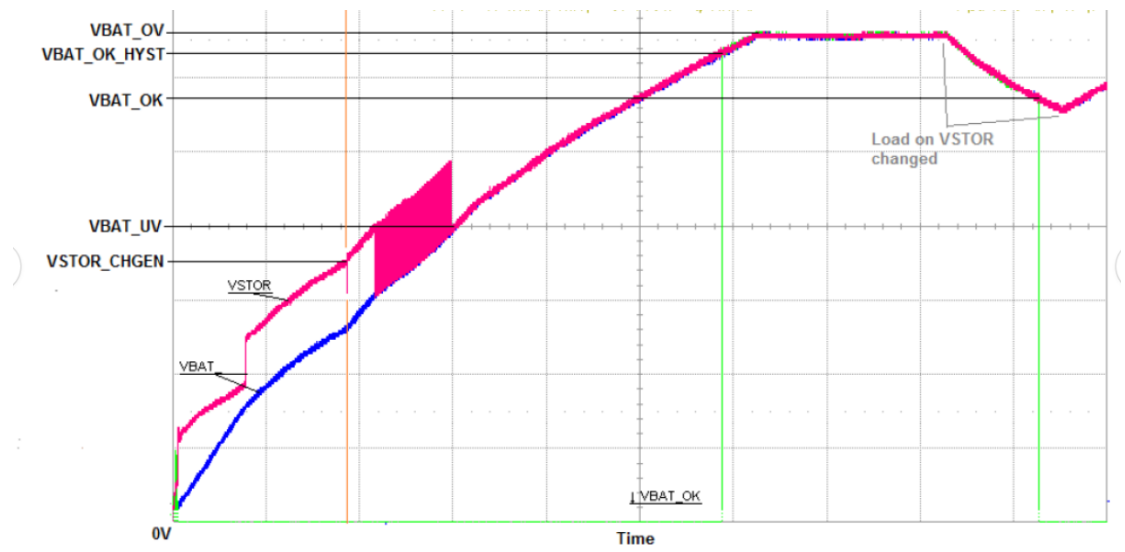

Data collected from 15 mins testing:

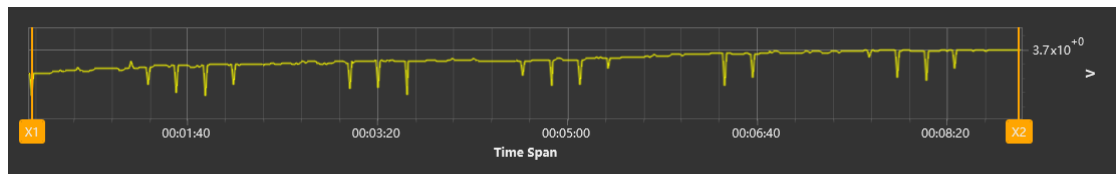

Time :	X1 Marker :	Measurement between Markers (X2-X1)				X2 Marker :
Measurement Value (V) :	00:00:00:18.022	Min :	Max :	Average :	Delta :	00:00:08:57.627
	3.668	3.668	3.7	3.6931	0.032	3.7